

Islamic University of Technology
Department of Electrical and Electronic Engineering (EEE)
Digital Electronics and Pulse Techniques(EEE 4484)

Lab-5

Necessary concepts which will be required to perform the examples and exercises:

- ⇒ **Signal**(s) are like physical wires.
- ⇒ **std_logic_vector** is just a vector (or, array/collection) of **std_logic** elements.
- ⇒ **others => '0'** is used to set/initialize all the elements of an array to **'0'**
- ⇒ **clk'event and clk = '1'** is used to indicate the *rising edge* of the clock signal.

There is an alternative statement

```
if (rising_edge = clk) then
```

```
...
```

```
...
```

- ⇒ **x"000000"** refers to hexadecimal in VHDL and that consists of 24 bits.

Example-1

4 to 1 Multiplexer:

 


Figure 1. 4 to 1 Multiplexer

Source code:

```
library ieee;
use ieee.std_logic_1164.all;
entity mux4_to_1 is

    port (

        I0 : in     std_logic;
        I1 : in     std_logic;
        I2 : in     std_logic;
        I3 : in     std_logic;
        sel : in     std_logic_vector (1 downto 0);
        output : out std_logic

    );

end entity;

architecture behavioral of mux4_to_1 is

begin

    process(sel)          -- process and sensitivity list
    begin

        case sel is

            when "00" => output <= I0;
            when "01" => output <= I1;
            when "10" => output <= I2;
            when others => output <= I3;

        end case;

    end process;

end architecture behavioral;
```

Test-bench code:

```
library ieee;
use ieee.std_logic_1164.all;

entity tb_mux4_to_1 is
end tb_mux4_to_1;

architecture behavioral of tb_mux4_to_1 is

    component mux4_to_1
    port (
        I0 : in     std_logic;
        I1 : in     std_logic;
        I2 : in     std_logic;
        I3 : in     std_logic;

        sel : in     std_logic_vector (1 downto 0);
        output : out std_logic
    );

    end component;

    signal tb_I0, tb_I1, tb_I2, tb_I3 : std_logic := '0';
    signal tb_sel : std_logic_vector (1 downto 0) := (others => '0');
```

```

    signal tb_output : std_logic;

begin

    uut: mux4_to_1 port map (
        I0 => tb_I0,
        I1 => tb_I1,
        I2 => tb_I2,
        I3 => tb_I3,
        sel => tb_sel,
        output => tb_output
    );

    -- stimulus process

    stim_process: process
    begin
        wait for 50 ns;

        tb_sel <= "00";
        tb_I0 <= '1'; tb_I1 <= '0'; tb_I2 <= '1'; tb_I3 <= '1';

        wait for 50 ns;
        tb_sel <= "01";

        wait for 50 ns;
        tb_sel <= "10";

        wait for 50 ns;
        tb_sel <= "11";

        wait for 50 ns;
        tb_I0 <= '0'; tb_I1 <= '1'; tb_I2 <= '0'; tb_I3 <= '0';
        tb_sel <= "11";

        wait for 50 ns;

    end process;
end architecture behavioral;

```

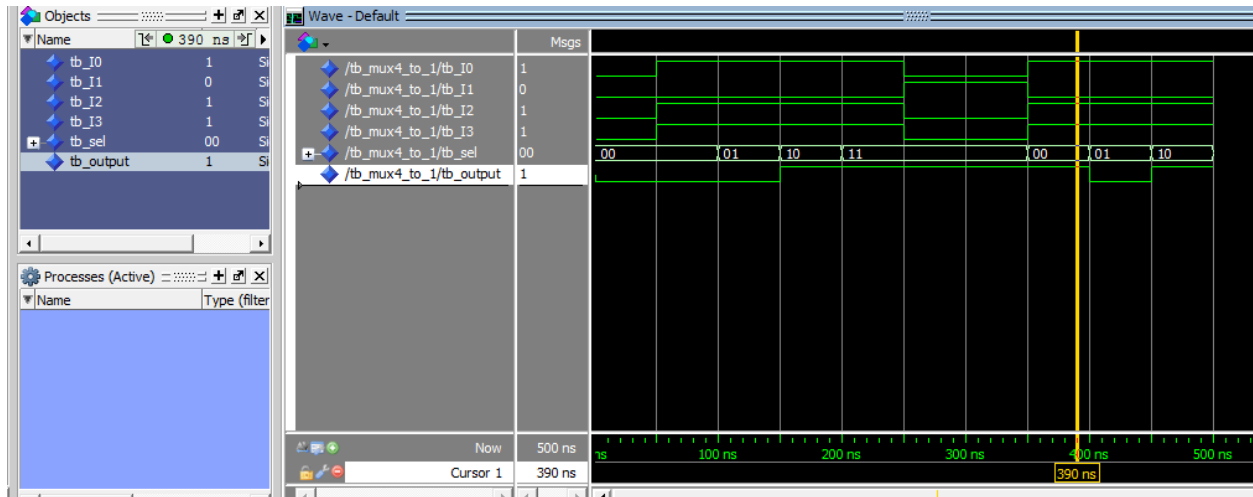


Figure 2. Simulation result (timing diagram) of the multiplexer testbench

Example-2

D Flip-Flop:

In general, we define a *synchronous sequential circuit*, or just *sequential circuit* as a circuit with m inputs, n outputs, and a distinguished *clock* input.

 


Figure 3. D Flip-Flop

Source code:

```
library ieee;
use ieee.std_logic_1164.all;

entity d_flipflop is
    port (
        clk : in  std_logic;
        D   : in  std_logic;
        Q   : out std_logic
    );
end entity;

architecture behavioral of d_flipflop is
begin
    process (clk, D)
    begin
        if (clk'event and clk = '1') then
            Q <= D;
        end if;
    end process;
end architecture behavioral;
```

Test-bench code:

```
library ieee;
use ieee.std_logic_1164.all;

entity tb_d_flipflop is
end tb_d_flipflop;

architecture behavioral of tb_d_flipflop is

    component d_flipflop
        port (
```

```

        clk : in    std_logic;
        D   : in    std_logic;
        Q   : out   std_logic
    );
    end component;

    signal clk      : std_logic;
    signal tb_D     : std_logic;
    signal tb_Q     : std_logic;

    constant clk_period : time := 100 ns; -- period of the clock

begin

    uut: d_flipflop port map(
        clk => clk,
        D  => tb_D,
        Q  => tb_Q
    );

    -- clock process
    clk_process: process
    begin
        clk <= '0';
        wait for clk_period/2;

        clk <= '1';
        wait for clk_period/2;
    end process;

    -- stimulus process
    stim_process: process
    begin
        wait for 50 ns;
        tb_D <= '0';

        wait for 50 ns;
        tb_D <= '1';

        wait for 50 ns;
        tb_D <= '0';

    end process;

end architecture behavioral;

```


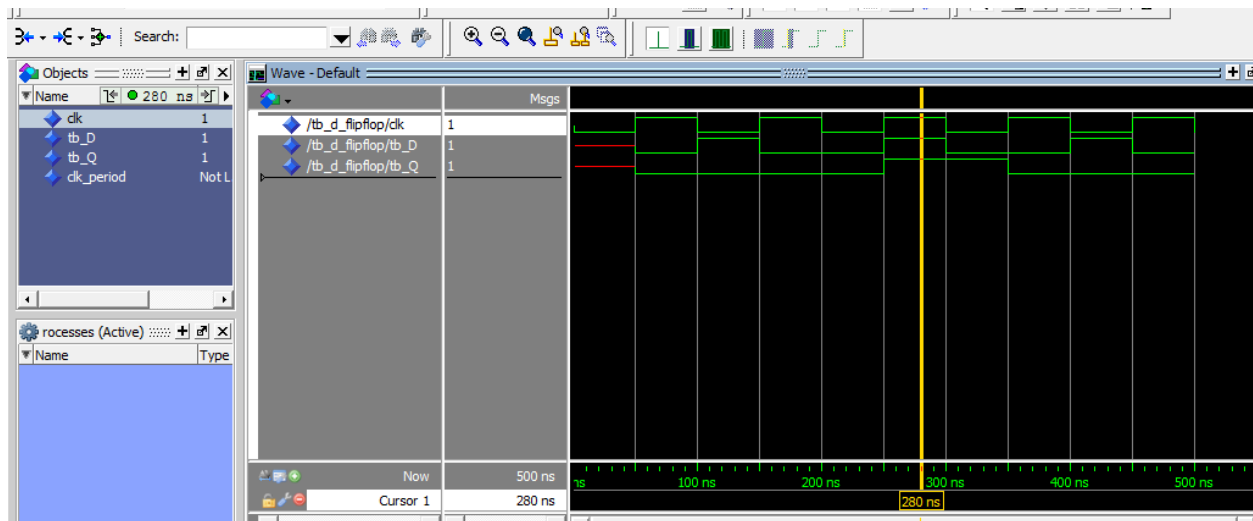


Figure 4. Simulation result (timing diagram) of the D-flipflop testbench

 Example-3

A binary encoder has $2n$ input lines and n output lines, hence it encodes the information from $2n$ inputs into an n -bit code. From all the input lines, only one of an input line is activated at a time, and depending on the input line, it produces the n bit output code.

Depending on the number of input lines, digital or binary encoders produce the output codes in the form of 2 or 3 or 4 bit codes.



(a)

Input				Output	
A[3]	A[2]	A[1]	A[0]	B[1]	B[0]
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

(b)

Figure 5. 4 to 2 Encoder (a) Block Diagram (b) Truth Table

Source code:

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity encoder is
  port(
    A: in STD_LOGIC_VECTOR(3 downto 0);
    B: out STD_LOGIC_VECTOR(1 downto 0)
  );
end encoder;

architecture behavioral of encoder is
begin
  process(a)
  begin
    if (A = "1000") then
      B <= "00";
    elsif (A = "0100") then
      B <= "01";
    elsif (A = "0010") then

```

```

        B <= "10";
    elsif (A = "0001") then
        B <= "11";
    else
        B <= "ZZ";
    end if;
end process;

end architecture behavioral;

```

Test-bench code:

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_encoder IS
END tb_encoder;

ARCHITECTURE behavioral OF tb_encoder IS

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT encoder
PORT(
    A : IN std_logic_vector(3 downto 0);
    B : OUT std_logic_vector(1 downto 0)
);
END COMPONENT;

--Inputs
signal tb_A : std_logic_vector(3 downto 0) := (others => '0');
--Outputs
signal tb_B : std_logic_vector(1 downto 0);

BEGIN

-- Instantiate the Unit Under Test (UUT)
uut: encoder PORT MAP (
    A => tb_A,
    B => tb_B
);

-- Stimulus process
stim_proc: process
begin
-- hold reset state for 100 ns.
    wait for 100 ns;
    tb_A <= "0000";

    wait for 100 ns;
    tb_A <= "0001";

    wait for 100 ns;
    tb_A <= "0010";

    wait for 100 ns;
    tb_A <= "0100";

    wait for 100 ns;
    tb_A <= "1000";

    wait;
end process;

END architecture behavioral;

```

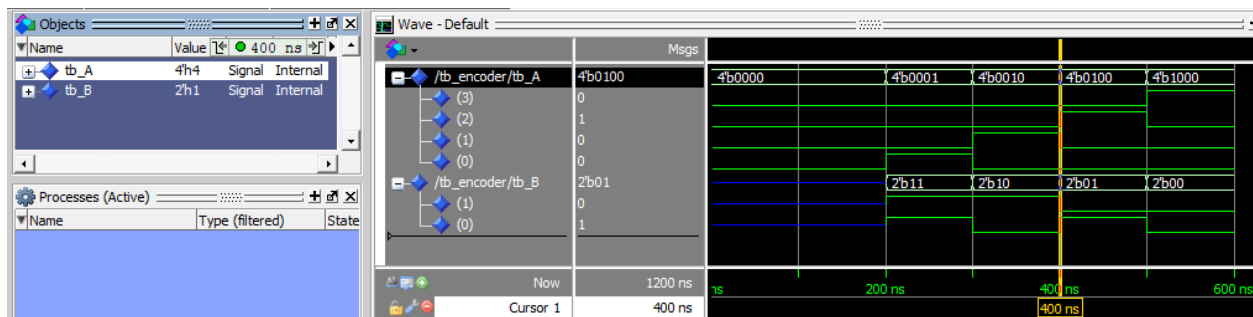


Figure 6. Simulation result (timing diagram) of the 4 to 2 Encoder testbench

Home tasks (Implement in VHDL. Compile and simulate with Modelsim)

1. Design a full-adder circuit. Then simulate and verify with testbench.
2. Design a 1 to 8 demultiplexer. Then simulate and verify with testbench.
3. Design a 4-bit Arithmetic Logic Unit (ALU) which can perform addition, subtraction, AND, OR operation between two numbers. Try to simulate with testbench.
4. Design a synchronous 5-bit shift register (use a input clock for synchronization). Then simulate and verify with testbench providing different combinations.