

Islamic University of Technology (IUT)

Organisation of Islamic Cooperation (OIC)

Department of Electrical and Electronic Engineering
Electronics Laboratory

Name: Student No..... Section and Group.....

Course: **EEE 4484 (Digital Electronics and Pulse Techniques Lab)**





Experiment no.: 02

Name of the experiment: Study of wave shapes different types of clipping and clamping circuits using PSIM.

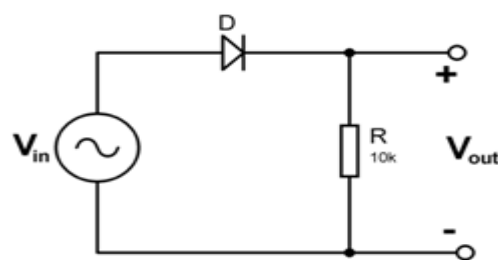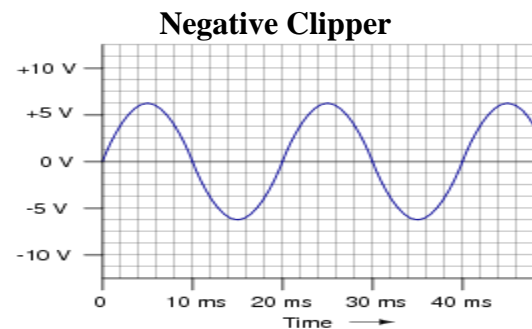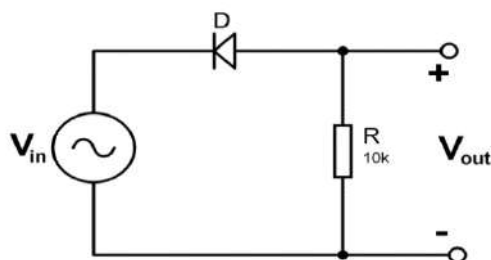
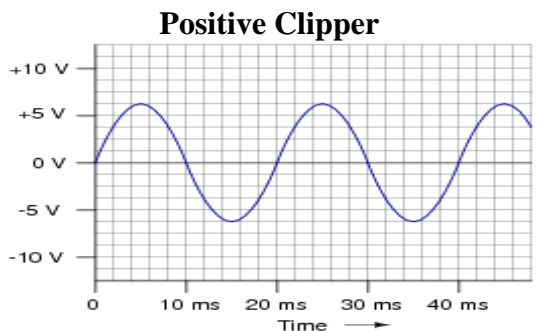
Part A: To construct the clipping circuits and observe its corresponding wave shapes.

Clipper circuit have the ability to “clip” off a portion of the input signal without distorting the remaining part of the alternating waveform. The half-wave rectifier of is an example of the simplest form of diode clipper - one resistor and diode. Depending on the orientation of the diode, the positive or negative region of the input signal is “clipped” off. There are two general categories of clippers: *series* and *parallel*. The series configuration is defined as one where the diode is in series with the load, while the parallel variety has the diode in a branch parallel to the load.

Series Clipper Circuit (with Diode and Resistor):



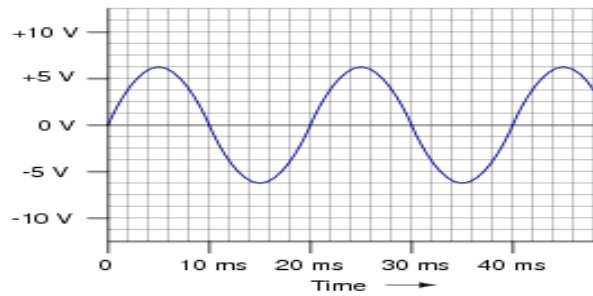
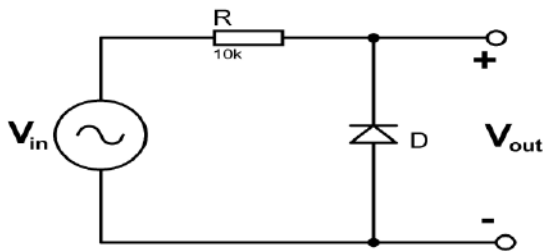
Parallel Clipper Circuit (with Diode and Resistor):





Biased Series Clipper Circuit (with Diode and Resistor):

- Take DC voltage as 2V/ 3V

Positive Clipper

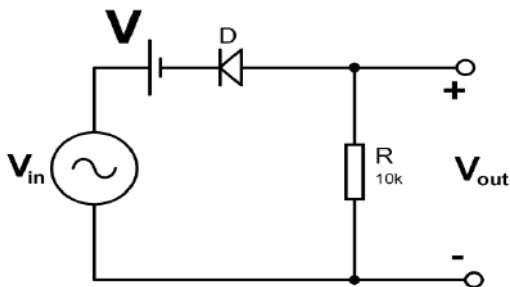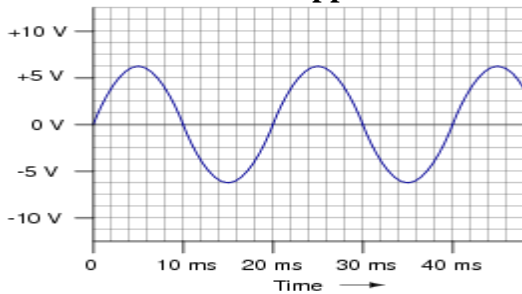


Negative Clipper

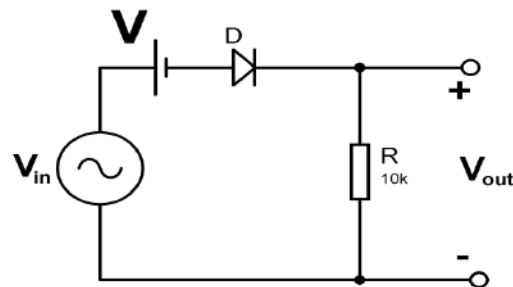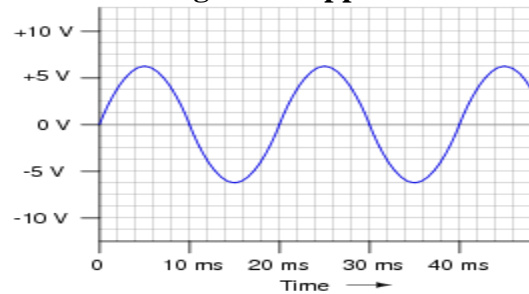




Biased Parallel Clipper Circuit (with Diode and Resistor):

Positive Clipper


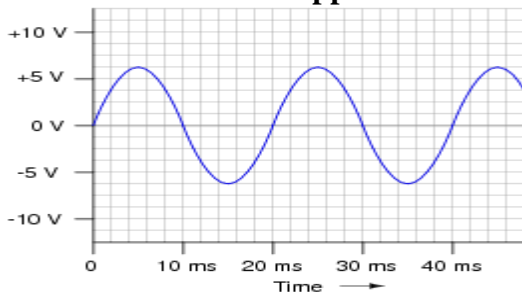


Negative Clipper

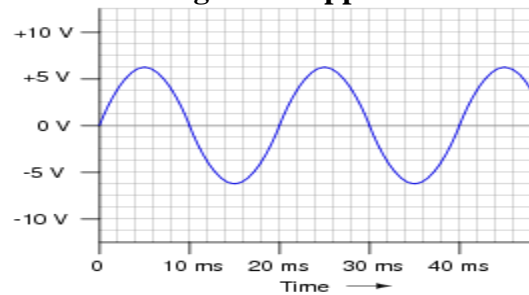

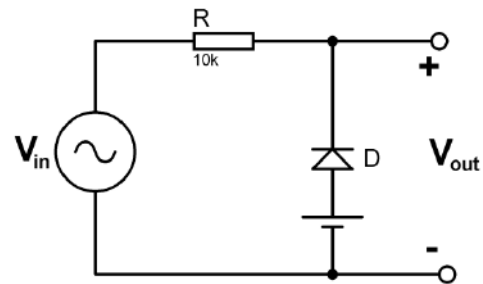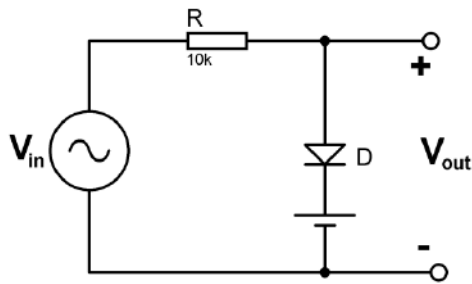

Combined

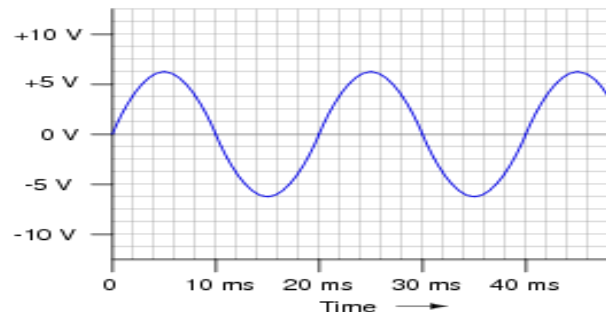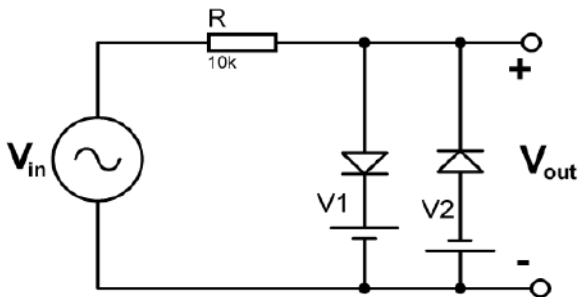



Part B: To construct the clamping circuits and observe its corresponding wave shapes.

Clamping circuit will “clamp” a signal to a different dc level. The network must have a capacitor, a diode, and a resistive element, but it can also employ an independent dc supply to introduce an additional shift. The magnitude of R and C must be chosen such that the time constant RC is large enough to ensure that the voltage across the capacitor does not discharge significantly during the interval the diode is nonconducting.



Series clamping Circuit (with Diode and Resistor):





- Take DC voltage as 2V/ 3V and resistance as 1000k to observe the outputs properly.
- Take the DC offset of square wave as -5V and Peak to peak voltage as 10V.

Positive clamper

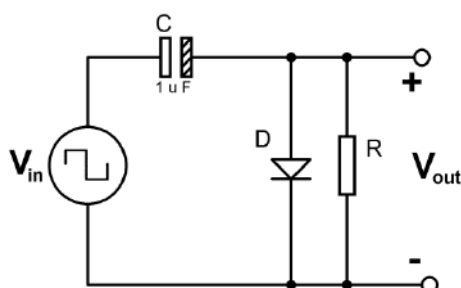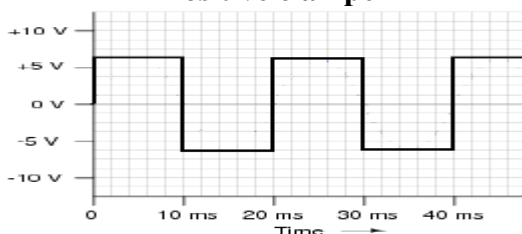

Negative clamper

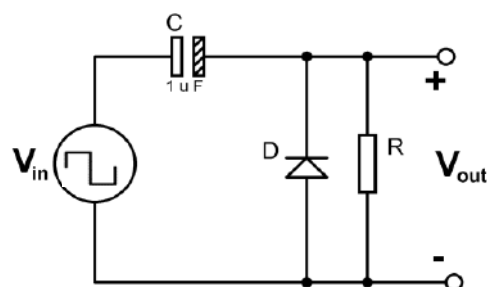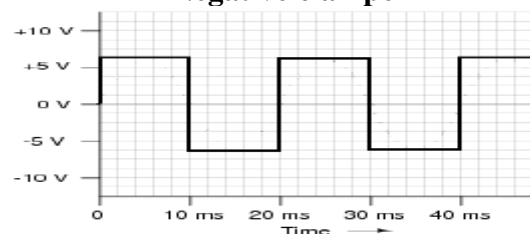


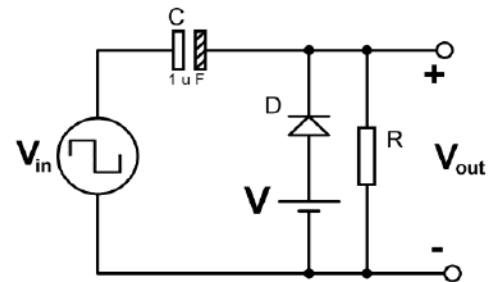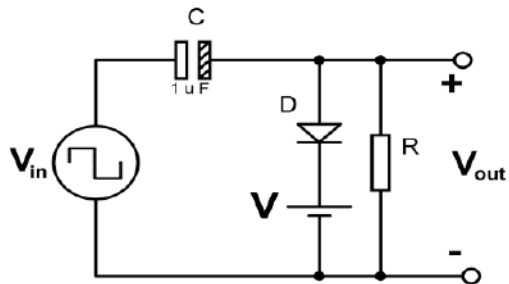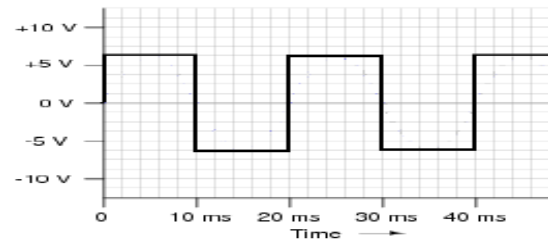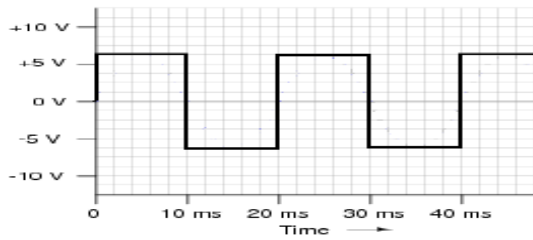


Assignments:

Construct the following circuits. Give suitable values for a sinusoidal input and observe the output voltage waveforms.


1.

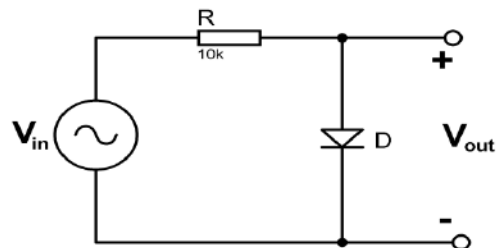


2.

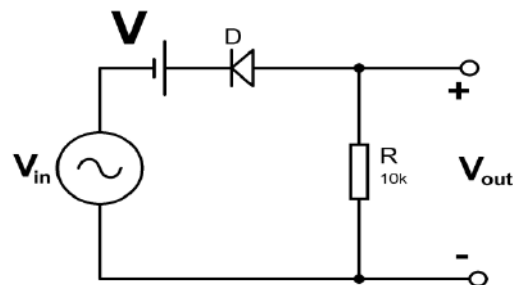


3.

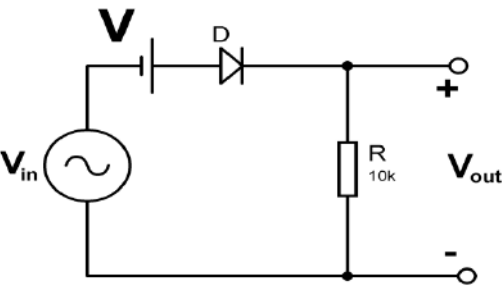


4.

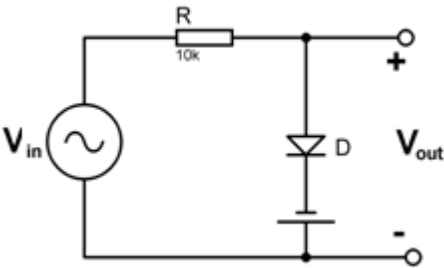

5.

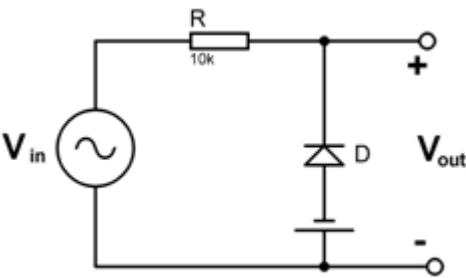

6.

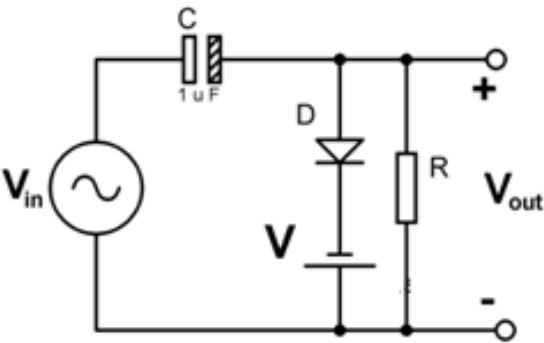

7.

